

EE310, Electronic Devices and Circuits I

Lecture Slides

Instructor:
Prof. Chu Ryang Wie

EE310 – Chapter 1

Introduction to Electronics

Lecture Slides

Instructor:


Prof. Chu Ryang Wie

1.1 Signal Source

(a) Thévenin Form



(b) Norton form

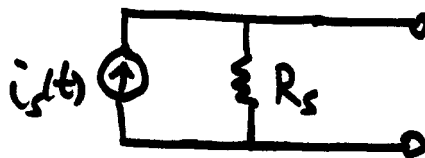

1.1 For the signal-source representations shown in Figs. 1.1(a) and 1.1(b), what are the open-circuit output voltages that would be observed? If, for each, the output terminals are short-circuited (i.e., wired together), what current would flow? For the representations to be equivalent, what must the relationship be between v_s , i_s , and R_s ?

Sol) ; i) Open Circuit voltage: (a) $V_{oc} = V_s$ (b) $V_{oc} = i_s R_s$

ii) Short circuit current: (a) $i_{sc} = \frac{V_s}{R_s}$ (b) $i_{sc} = i_s$

iii) For Thévenin (a) and Norton (b) to represent the same Source: V_{oc} and i_{sc} must be the same!

$$\therefore V_{oc} = V_s = i_s R_s \quad i_{sc} = \frac{V_s}{R_s} = i_s$$

1.2 A signal source has an open-circuit voltage of 10 mV and a short-circuit current of 10 μ A. What is the source resistance?

Sol) $V_{oc} = 10 \text{ mV}$ $i_{sc} = 10 \mu\text{A}$ $R_s = ?$

$$i_{sc} = \frac{V_s}{R_s} = \frac{10 \text{ mV}}{R_s} = 10 \mu\text{A}$$

$$\therefore R_s = \frac{10 \text{ mV}}{10 \mu\text{A}} = 1 \text{ k}\Omega$$

1.2 Frequency Spectrum

$$V_a(t) = V_a \sin \omega t$$

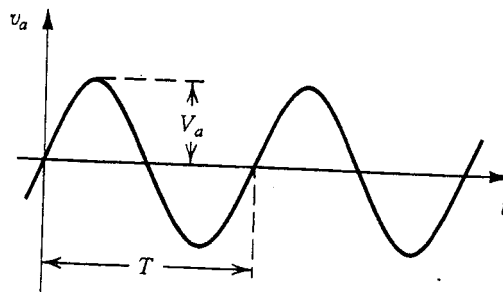


FIGURE 1.3 Sine-wave voltage signal of amplitude V_a and frequency $f = 1/T$ Hz. The angular frequency $\omega = 2\pi f$ rad/s.

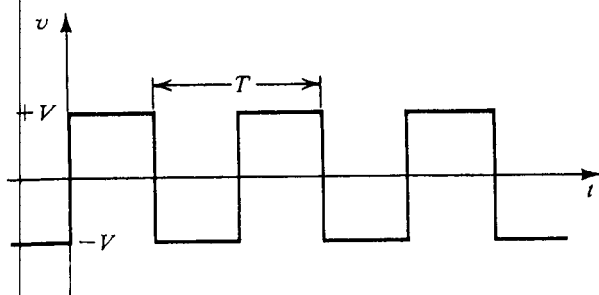


FIGURE 1.4 A symmetrical square-wave signal of amplitude V .

Fourier Expansion:

$$V(t) = \frac{4V}{\pi} \left(\sin \omega_0 t + \frac{1}{3} \sin 3\omega_0 t + \frac{1}{5} \sin 5\omega_0 t + \dots \right)$$

$$\omega_0 = \frac{2\pi}{T}$$

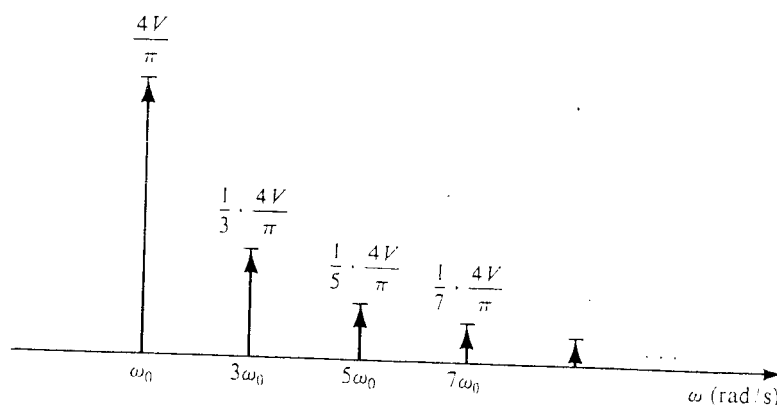


FIGURE 1.5 The frequency spectrum (also known as the line spectrum) of the periodic square wave of Fig. 1.4.

- 1.6 When the square-wave signal of Fig. 1.4, whose Fourier series is given in Eq. (1.2), is applied to a resistor, the total power dissipated may be calculated directly using the relationship $P = 1/T \int_0^T (v^2/R) dt$ or indirectly by summing the contribution of each of the harmonic components, that is, $P = P_1 + P_3 + P_5 + \dots$, which may be found directly from rms values. Verify that the two approaches are equivalent. What fraction of the energy of a square wave is in its fundamental? In its first five harmonics? In its first seven? First nine? In what number of harmonics is 90% of the energy? (Note that in counting harmonics, the fundamental at ω_0 is the first, the one at $2\omega_0$ is the second, etc.)

$$\begin{aligned}
 \text{Sol) Power} &= \frac{1}{T} \int_0^T \frac{v^2}{R} dt, \quad v^2 = \left(\frac{4V}{\pi}\right)^2 \left(\sin^2 \omega_0 t + \frac{1}{9} \sin^2 3\omega_0 t + \frac{1}{25} \sin^2 5\omega_0 t + \dots \right) \\
 &= \frac{1}{T} \left(\frac{4V}{\pi}\right)^2 \cdot \frac{T}{2R} \left(1 + \frac{1}{9} + \frac{1}{25} + \frac{1}{49} + \dots \right) \\
 &= \frac{8}{\pi^2} \frac{V^2}{R} \sum_{n=1}^{\infty} \frac{1}{n^2} \qquad \sum_{n=1}^{\infty} \frac{1}{n^2} = \frac{\pi^2}{6} \\
 &= \frac{V^2}{R}
 \end{aligned}$$

$$P = P_1 + P_3 + P_5 + P_7 + \dots$$

$$\frac{P_1}{P} = \frac{1}{\sum \frac{1}{n^2}} = \frac{1}{\pi^2/6} = 0.81$$

$$\frac{P_1 + P_3 + P_5}{P} = \frac{1 + \frac{1}{9} + \frac{1}{25}}{\sum \frac{1}{n^2}} = \frac{1.151}{\pi^2/6} = 0.93$$

$$\frac{P_1 + P_3}{P} = \frac{1 + \frac{1}{9}}{\pi^2/6} = 0.90$$

1.4 Amplifier

Gain:

$$v_o(t) = A v_i(t)$$

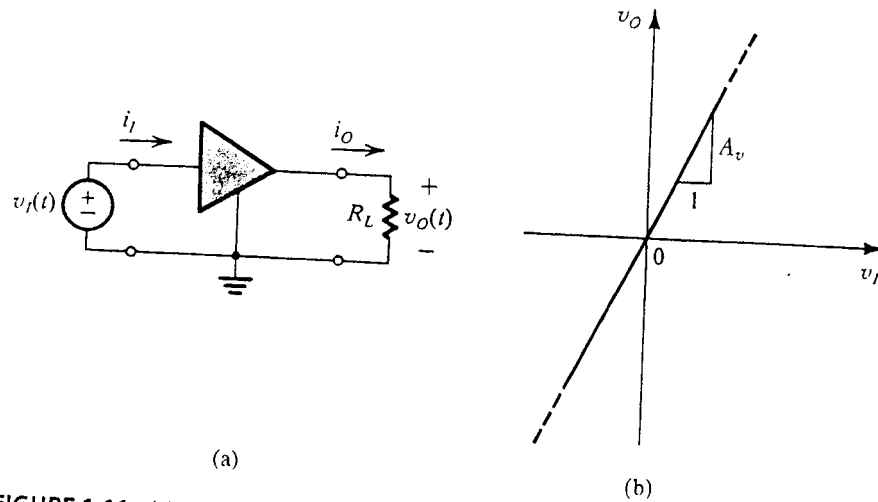


FIGURE 1.11 (a) A voltage amplifier fed with a signal $v_i(t)$ and connected to a load resistance R_L . (b) Transfer characteristic of a linear voltage amplifier with voltage gain A_v .

$$A_v = \frac{v_o}{v_i} \quad [V/V] \quad \leftrightarrow \quad 20 \log |A_v| \quad [dB]$$

$$A_i = \frac{i_o}{i_i} \quad [A/A] \quad \leftrightarrow \quad 20 \log |A_i| \quad [dB]$$

$$A_p = \frac{P_o}{P_i} \quad [W/W] = \frac{v_o i_o}{v_i i_i} \quad \leftrightarrow \quad 10 \log |A_p| \quad [dB]$$


1.8 An amplifier has a voltage gain of 100 V/V and a current gain of 1000 A/A. Express the voltage and current gains in decibels and find the power gain.

Sol) $A_v = 100 \text{ V/V} \quad \leftrightarrow \quad 20 \log 100 = 40 \text{ dB}$

$$A_i = 1000 \text{ A/A} \quad \leftrightarrow \quad 20 \log 1000 = 60 \text{ dB}$$

$$A_p = A_v \cdot A_i = 10^2 \cdot 10^3 \text{ W/W} \quad \leftrightarrow \quad 10 \log 10^5 = 50 \text{ dB}$$

Amplifier Power Supplies

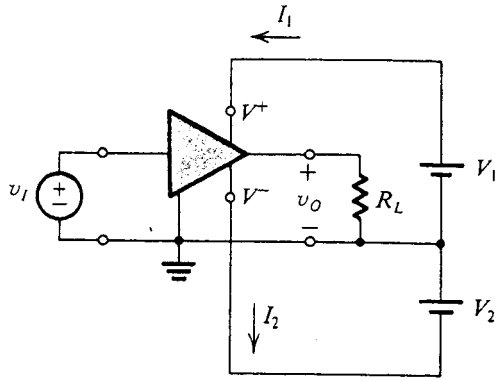

$$P_{dc} = V_1 I_1 + V_2 I_2$$

$$P_{dc} + P_I = P_L + P_{dissipated}$$

- 1.9 An amplifier operating from a single 15-V supply provides a 12-V peak-to-peak sine-wave signal to a 1-k Ω load and draws negligible input current from the signal source. The dc current drawn from the 15-V supply is 8 mA. What is the power dissipated in the amplifier, and what is the amplifier efficiency?

Sol) DC supply: $V_{dc} = 15\text{-V}$ $I_{dc} = 8\text{ mA}$

input: $i_i \approx 0$

output: $v_o = 6\text{ V sin}\omega t$ $R_L = 1\text{-k}\Omega$

$$P_{diss} = P_{dc} + P_I - P_L$$

$$P_{dc} = V_{dc} I_{dc} = 15\text{ V} \cdot 8\text{ mA} = 120\text{ mW}$$

$$P_I \approx 0$$

$$P_L = \frac{V_{o,rms}^2}{R_L} = \frac{(6/\sqrt{2})^2}{1\text{-k}\Omega} = 18\text{ mW}$$


$$\therefore P_{diss} = 120 + 0 - 18 = 102\text{ mW}$$

$$\text{Efficiency } \eta = \frac{P_L}{P_{dc}} \times 100 = \frac{18}{120} \times 100 = 15\%$$

1.5 Amplifier Circuit Models


- Voltage Amp

-1.6-

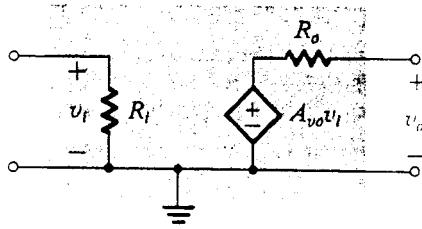


(a)

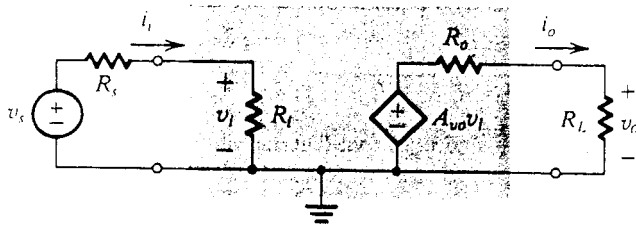Open Circuit: $v_o = A_{vo} v_i$
 $\therefore \text{Gain} = \frac{v_o}{v_i} \equiv A_{vo}$



(b)

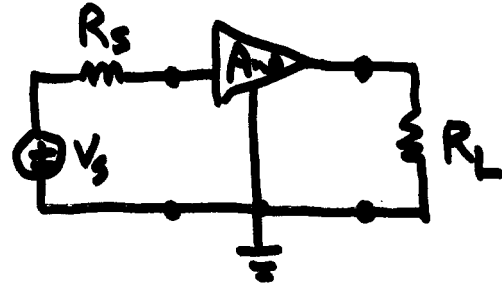

Now, with R_L : $v_o = A_{vo} v_i \frac{R_L}{R_L + R_o}$

$\therefore \text{Gain} = \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o} \equiv A_v$

For a Large A_v , make $R_L \gg R_o$

1.12 The output voltage of a voltage amplifier has been found to decrease by 20% when a load resistance of $1 \text{ k}\Omega$ is connected. What is the value of the amplifier output resistance?

sol) After $R_L = 1 \text{ k}\Omega$ is connected,

$A_v = A_{vo} \frac{1 \text{ k}}{1 \text{ k} + R_o} = 0.8 A_{vo} \quad \therefore R_o = 0.25 \text{ k}$

1.13 An amplifier with a voltage gain of +40 dB, an input resistance of 10 k Ω , and an output resistance of 1 k Ω is used to drive a 1-k Ω load. What is the value of A_{vo} ? Find the value of power gain in dB.

Amp: 40 dB, $R_i = 10 \text{ k}\Omega$ $R_o = 1 \text{ k}\Omega$

Load: $R_L = 1 \text{ k}\Omega$

Sol) $40 \text{ dB} = 20 \log |A_{vo}| \therefore A_{vo} = 100 \text{ V/V}$

Power Gain = $\frac{P_L}{P_i}$ where $\begin{cases} P_L = \frac{V_o^2}{R_L} \\ P_i = \frac{V_i^2}{R_i} \end{cases}$

$\therefore A_p = \frac{P_L}{P_i} = \left(\frac{V_o}{V_i}\right)^2 \frac{R_i}{R_L}$

$\frac{V_o}{V_i} = A_{vo} \frac{R_L}{R_L + R_o} = 100 \frac{1 \text{ k}}{1 \text{ k} + 1 \text{ k}} = 50$

$A_p = (50 \frac{\text{V}}{\text{V}})^2 \frac{10 \text{ k}}{1 \text{ k}} = 25,000 \frac{\text{W}}{\text{W}} = 10 \log(25,000) \text{ dB}$
 $= 43.98 \text{ dB}$


Overall Voltage Gain $\equiv \frac{V_o}{V_s} = V_s \rightarrow V_o$

$V_i = V_s \frac{R_i}{R_i + R_s}$

$\frac{V_o}{V_s} = \frac{V_o}{V_i} \frac{V_i}{V_s} = A_v \frac{R_i}{R_i + R_s} = A_{vo} \frac{R_L}{R_L + R_o} \frac{R_i}{R_i + R_s}$



EXAMPLE 1.3

1.5.2 Cascaded Amplifiers

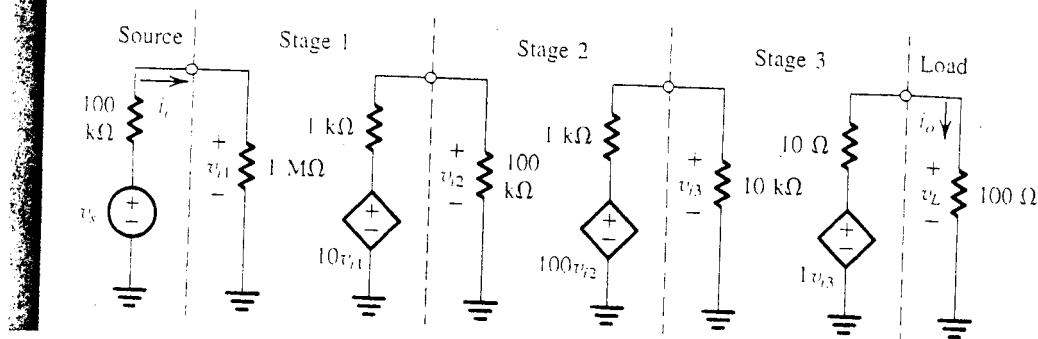

1.16 (a). Model the three-stage amplifier of Example 1.3 (without the source and load) using the voltage amplifier model. What are the values of R_i , A_{v0} , and R_o ?

Sol)

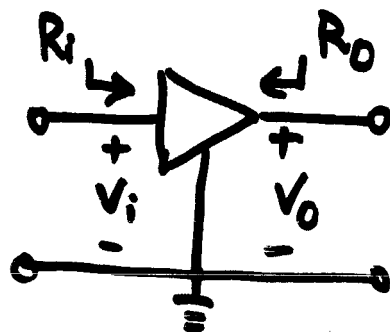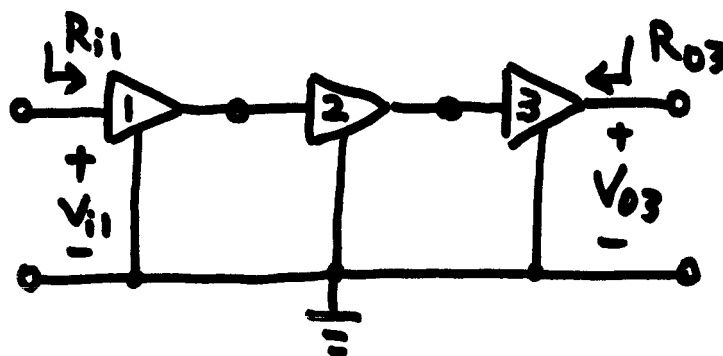

$$R_i = R_{i1} = 1 \text{ M}\Omega$$

$$R_o = R_{o3} = 10 \Omega$$

$$\begin{aligned} A_{v0} &= \frac{V_o}{V_i} = \frac{V_{o3}}{V_{i1}} \\ &= \frac{V_{o3}}{V_{i3}} \cdot \frac{V_{i3}}{V_{i2}} \cdot \frac{V_{i2}}{V_{i1}} \\ &= 1 \times 90.9 \times 9.9 \\ &= 900.1 \text{ V/V} \end{aligned}$$

From Exa 1.3

$$\frac{V_{o3}}{V_{i3}} = 1 \text{ V/V}$$

$$\frac{V_{i3}}{V_{i2}} = 100 \cdot \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 1 \text{ k}\Omega} = 90.9 \text{ V/V}$$

$$\frac{V_{i2}}{V_{i1}} = 10 \cdot \frac{100 \text{ k}\Omega}{100 \text{ k}\Omega + 1 \text{ k}\Omega} = 9.9 \text{ V/V}$$

- 1.18 Consider the transconductance amplifier whose model is shown in the third row of Table 1.1. Let a voltage signal-source v_s with a source resistance R_s be connected to the input and a load resistance R_L be connected to the output. Show that the overall voltage-gain is given by

$$\frac{v_o}{v_s} = G_m \frac{R_i}{R_i + R_s} (R_o \parallel R_L)$$

Sol) Transconductance Amplifier
With Load, Source



$$V_i = V_s \frac{R_i}{R_i + R_s}$$

$$V_o = G_m V_i \cdot (R_o \parallel R_L)$$


Therefore,

$$\text{the Overall Voltage Gain} = \frac{V_o}{V_s}$$

$$\frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s} = G_m (R_o \parallel R_L) \cdot \frac{R_i}{R_i + R_s}$$



1.6 FREQUENCY RESPONSE OF AMPLIFIERS

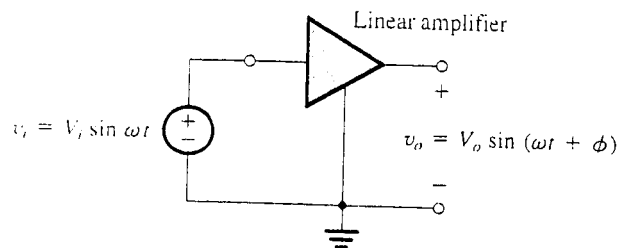


Transfer Function $T(\omega)$

$$|T(\omega)| = \frac{V_o}{V_i}$$

$$\angle T(\omega) = \phi$$

1.6.2 Amplifier Bandwidth

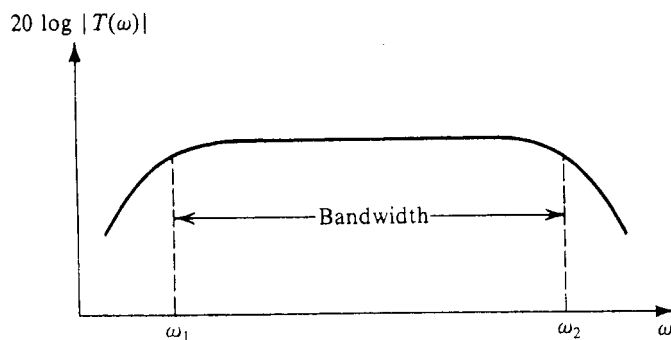


$$T(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

OR,

$$T(s) = \frac{V_o(s)}{V_i(s)}, \text{ where}$$

$s \equiv j\omega = \text{Complex Freq.}$

1.6.4 Single-Time-Constant Networks

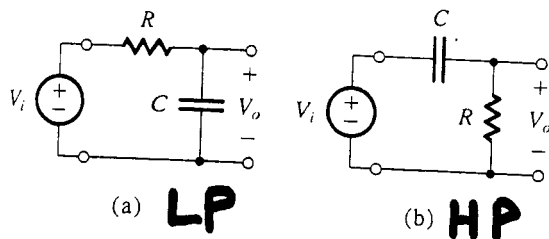

(a) Low-Pass : $\frac{V_o}{V_i} = \frac{1/sC}{1/sC + R} = \frac{1}{1 + sCR} \approx \frac{1}{1 + \frac{s}{\omega_0}}$

where, $\omega_0 \equiv \frac{1}{CR}$

To account for DC gain, use K :

$$T(s) = \frac{K}{1 + \frac{s}{\omega_0}}$$

ex) $T(\omega=0) = K$ $T(\omega=\infty) = 0 \quad \therefore \text{LP}$

(b) High-Pass : $T(s) = \frac{V_o}{V_i} = \frac{K}{1 + \frac{\omega_0}{s}}$

ex) $T(\omega=0) = 0$ $T(\omega=\infty) = K \quad \therefore \text{HP}$

1.21 Consider a voltage amplifier having a frequency response of the low-pass STC type with a dc gain of 60 dB and a 3-dB frequency of 1000 Hz. Find the gain in dB at $f = 10$ Hz, 10 kHz, 100 kHz, and 1 MHz.

Sol) $K = 60 \text{ dB} = 1000 \frac{V}{V}$, $f_{3\text{dB}} = 1 \text{ kHz}$ LP

Gain at $f = 10$, 10k, 100k, and 1MHz?

LP: $T(s) = \frac{K}{1 + \frac{s}{\omega_0}}$

At $\omega = \omega_0$,

$|T| = \frac{K}{\sqrt{2}}$, and

$20 \log |T| = 20 \log K - 3 \text{ dB}$

$\therefore \omega_0 = 2\pi f_{3\text{dB}}$

For $|s| = \omega \gg \omega_0$,

$|T(s)| \approx \frac{K}{|s/\omega_0|} = K \frac{\omega_0}{\omega}$

Gain $= 20 \log |T| \approx 20 \log K - 20 \log \frac{\omega}{\omega_0}$

ex)	$\omega \rightarrow 10 \times$	$100 \times$	$1000 \times$
	Gain $\rightarrow -20 \text{ dB}$	-40 dB	-60 dB

For $|s| = \omega \ll \omega_0$, $T(s) = K$

$\therefore f =$	$10 \text{ Hz} \ll 1 \text{ kHz} \ll$	10 kHz	100 kHz	1 MHz
Gain =	60 dB	57 dB	40 dB	20 dB
				0 dB

Note: Unity Gain Frequency ω_T : Gain = 0 dB at ω_T

Gain $= K \frac{\omega_0}{\omega_T} = 1 \therefore \omega_T = K \omega_0$

check $f_T = K f_{3\text{dB}} = 1000 \frac{V}{V} \cdot 1 \text{ kHz} = 1000 \text{ kHz}$